

Find i_o in the circuit of Fig. 4.19 using source transformation.

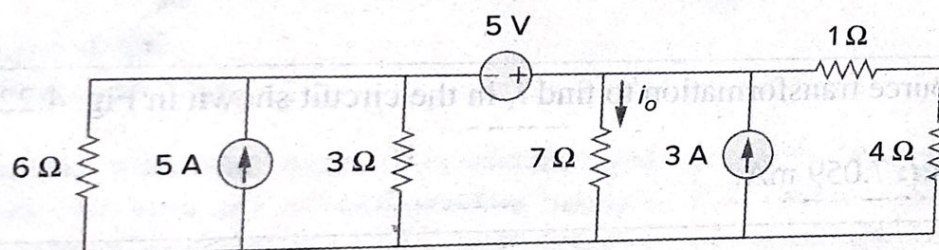


Figure 4.19
For Practice Prob. 4.6.

Answer: 1.78 A.

Practice Problem 4.6

